

CPLD 設計作業

銘傳大學電腦與通訊工程系

班 級	電通二乙
組 別	第 27 組
組員姓名/學號	05050032 陳韋濤
組員姓名/學號	05050536 陳奕璽
作業撰寫人	陳韋濤
授課教師	陳慶逸
實習成果	本次應繳作業共 <u>2</u> 題，完成 <u>2</u> 題
時 間	2017/12/1

第一題

問題描述: 實現一個 1Hz 頻率計數的 3 bits 計數器

程式碼:計數器

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
use ieee.std_logic_unsigned.all;
ENTITY aa IS
PORT(  x,CLK :IN STD_LOGIC;
       OP      :OUT std_logic_vector(2 downto 0));
END aa;

ARCHITECTURE a OF aa IS
BEGIN
PROCESS(clk)
variable present_state: std_logic_vector (2 downto 0);
    BEGIN
IF clk'event and clk='1' then
    CASE present_state IS
        WHEN "000" =>
            if x='1' then present_state:="001";
            else present_state:="111";
            end if;
        WHEN "001" =>
            if x='1' then present_state:="010";
            else present_state:="000";
            end if;
        WHEN "010" =>
            if x='1' then present_state:="011";
            else present_state:="001";
            end if;
        WHEN "011" =>
            if x='1' then present_state:="100";
            else present_state:="010";
            end if;
        WHEN "100" =>
```

```

        if x='1' then    present_state:="101";
        else present_state:="011";
        end if;
    WHEN "101" =>
        if x='1' then    present_state:="110";
        else present_state:="100";
        end if;
    WHEN "110" =>
        if x='1' then    present_state:="111";
        else present_state:="101";
        end if;
    WHEN "111" =>
        if x='1' then    present_state:="000";
        else present_state:="110";
        end if;
    WHEN others=>
        if x='1' then    present_state:="000";
        else present_state:="000";
        end if;
    END CASE;
end if;
op<= present_state;
END PROCESS;
END a;

```

1HZ 除頻

```

library ieee;
use ieee.std_logic_1164.all;

entity slowCLK is
    generic(divisor:integer:=500000000);
    port(   clockIN : in   std_logic;

           clockOUT: out std_logic);
end slowCLK;

architecture arch of slowCLK is

```

```

signal PULSE : std_logic;
begin
process(clockIN)
variable counter,divisor2 : integer range 0 to divisor;
begin
    divisor2:=divisor/2;
    if (clockIN 'event and clockIN ='1') then
        if counter = divisor then
            counter := 1;
        else
            counter := counter + 1;
        end if;
    end if;
    if (clockIN 'event and clockIN ='1') then
        if (( counter= divisor2) or (counter = divisor))then
            PULSE <= not PULSE ;
        end if;
    end if;
    clockOUT <= PULSE ;
end process;
end arch;

```


模擬結果:

逆時針:<https://www.youtube.com/watch?v=8PIzlaCHh4s>

順時針: https://www.youtube.com/watch?v=H_QdpNDrE-U

第二題

題目： 試實現下面之 Mealy 狀態機

 

程式碼:

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
use ieee.std_logic_unsigned.all;

ENTITY dd IS
PORT(CLK  :IN STD_LOGIC;
      X    :IN STD_LOGIC;
      op   :OUT STD_LOGIC);
END dd;

ARCHITECTURE a OF dd IS
TYPE State IS (s0,s1,s2,s3,s4);
SIGNAL present_state : State;
SIGNAL next_state: State;
BEGIN
    state_comp: PROCESS(present_state)
```

```
BEGIN
CASE present_state IS
WHEN s0 =>
    IF X = '0' THEN
        next_state <= s0;
    ELSE
        next_state <= s1;
    END IF;
    IF X = '0' THEN
        op <= '0';
    ELSE
        op <= '0';
    END IF;
WHEN s1 =>
    IF X = '0' THEN
        next_state <= s2;
    ELSE
        next_state <= s3;
    END IF;
    IF X = '0' THEN
        op <= '0';
    ELSE
        op <= '0';
    END IF;
WHEN s2 =>
    IF X = '0' THEN
```

```
        next_state <= s4;
    ELSE
        next_state <= s0;
    END IF;
    IF X = '0' THEN
        op <= '0';
    ELSE
        op <= '1';
    END IF;
    WHEN s3 =>
        IF X = '0' THEN
            next_state <= s1;
        ELSE
            next_state <= s2;
        END IF;
        IF X = '0' THEN
            op <= '1';
        ELSE
            op <= '1';
        END IF;
    WHEN s4 =>
        IF X = '0' THEN
            next_state <= s3;
        ELSE
            next_state <= s4;
        END IF;
```

```

IF X = '0' THEN

    op <= '1';

ELSE

    op <= '1';

END IF;

END CASE;

END PROCESS state_comp;


state_clocking: PROCESS (CLK)

BEGIN

    IF CLK'EVENT AND CLK = '1' THEN

        present_state <= next_state;

    END IF;

END PROCESS state_clocking;

END a;

```

