

CPLD 設計作業

銘傳大學電腦與通訊工程系

班 級	電通二乙
組 別	第 27 組
組員姓名/學號	陳韋濤 05050032
組員姓名/學號	陳奕璿 05050536
作業撰寫人	陳韋濤
授課教師	陳慶逸
實習成果	本次應繳作業共 <u>3</u> 題，完成 <u>3</u> 題
時 間	2017/10/20

第一題

問題描述: 使用 if-then-else 敘述


設計一個可以顯示數字 0-9, A 到 F 的七段顯示器解碼電路(共陽極), 並在 DE0

實驗板進行驗證


程式碼:


```
library ieee;
use ieee.std_logic_1164.all;
entity sevseg_UP1 is
port(  SW:in std_logic_vector(3 downto 0);
      HEX0_D:out std_logic_vector(0 to 6));
end sevseg_UP1;


architecture a of sevseg_UP1 is
begin
    process(SW)
begin
    if SW= "0000" then HEX0_D<="0000001";
    elsif SW="0001" then HEX0_D<="1001111";
    elsif SW="0010" then HEX0_D<="0010010";
    elsif SW="0011" then HEX0_D<="0000110";
    elsif SW="0100" then HEX0_D<="1001100";
    elsif SW="0101" then HEX0_D<="0100100";
    elsif SW="0110" then HEX0_D<="0100000";
    elsif SW="0111" then HEX0_D<="0001111";
    elsif SW="1000" then HEX0_D<="0000000";
    elsif SW="1001" then HEX0_D<="0000100";
    elsif SW="1010" then HEX0_D<="0001000";
    elsif SW="1011" then HEX0_D<="1100000";
    elsif SW="1100" then HEX0_D<="0110001";
    elsif SW="1101" then HEX0_D<="1000010";
    elsif SW="1110" then HEX0_D<="0110000";
    else HEX0_D<="0111000" ;
    end if;
    end process;
end a;
```

 



模 擬 結 果：

 


 


 


 


 


 


 


 


 


 


 

 

 


 

 

第二題

 問題描述：試完成下面的微分電路；其中 UP_out 為上緣微分，DN_out 為下緣微分，而 UD_out 為上下緣微分。



程式碼：

```
library ieee;
use ieee.std_logic_1164.all;


entity dd is
    port(A, CLK : in std_logic;
         UP ,DN ,UD      : out std_logic);
end dd;

architecture behavioral of dd is
    signal D0, D1: std_logic;
begin
    D_ff: process(CLK)
        begin
            if CLK'event and CLK='1' then
                D0 <= A;
                D1 <= D0;
            end if;
        end process D_ff;


    UP <= D0 AND (not D1);
    DN <= D1 and (not D0);
    UD <= D0 xor D1;
```

end behavioral;

模擬結果:

 

第三題

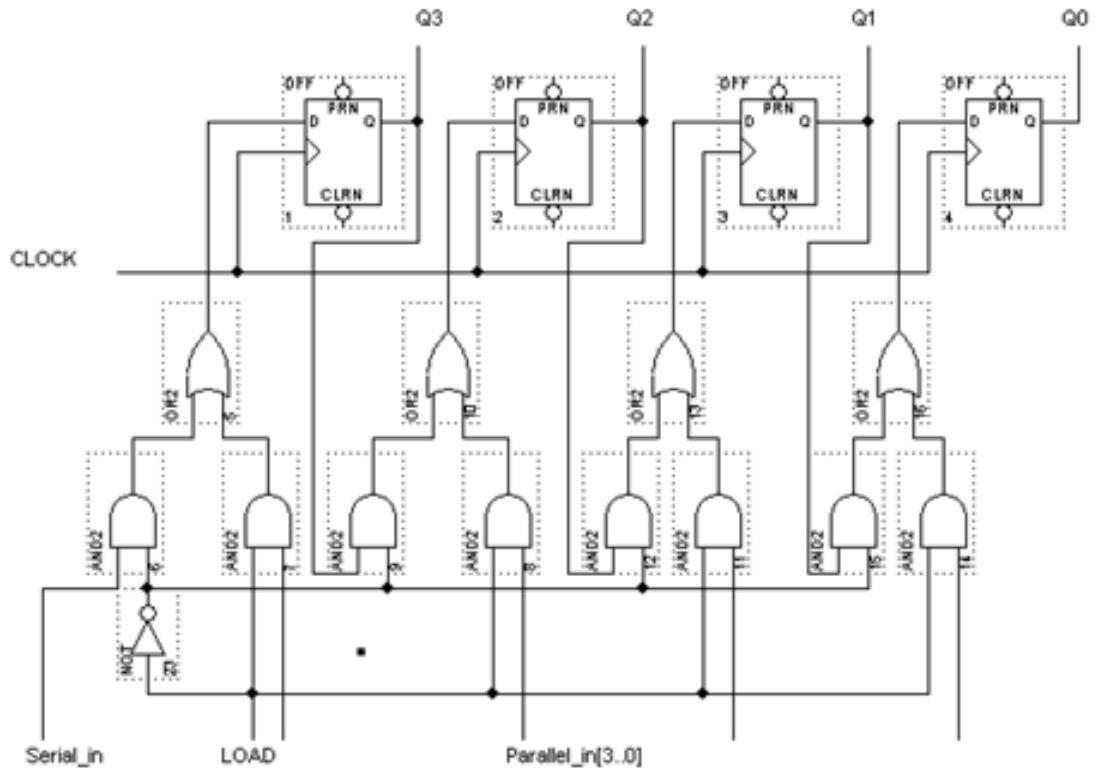

問題描述:

程式碼:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY abc IS
    PORT (Parallel_in : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
          Clock : IN STD_LOGIC;
          Serial_in : IN STD_LOGIC;
          LOAD:IN STD_LOGIC;
          Q : BUFFER STD_LOGIC_VECTOR(3 DOWNTO 0));
END abc;

ARCHITECTURE a OF abc IS
BEGIN
process
    begin
        wait until Clock'EVENT AND Clock = '1';
        if LOAD = '1' then
            Q <= Parallel_in;
        else
```

```

Q(0)<=Q(1);
Q(1)<=Q(2);
Q(2)<=Q(3);
Q(3)<=Serial_in;

end if;
end process;
END a;

```

模 擬 結 果 :

