

# CPLD 設計作業

銘傳大學電腦與通訊工程系

班 級	電通二乙
組 別	第 27 組
組員姓名/學號	陳韋濤/05050032
組員姓名/學號	陳奕璉/05050536
作業撰寫人	陳韋濤
授課教師	陳慶逸
實習成果	本次應繳作業共 <u>3</u> 題，完成 <u>3</u> 題
時 間	2017/12/08

## 第一題

- 問題描述： 利用階層式設計實現一個半加法器(h\_adder.vhd)

(互斥或閘: xor\_2.vhd, 及閘: and\_2.vhd)。

程式碼: h\_adder

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

ENTITY h_adder IS
PORT (  A,B : IN STD_LOGIC;
       Sum,Carry : out  STD_LOGIC);
END h_adder;
ARCHITECTURE a OF h_adder IS
    component and_2
        port ( A,B :in std_logic;
              Carry : out std_logic );
    end component;

    component xor_2
        port ( A,B :in std_logic;
              Sum :out std_logic );
    end component;

BEGIN
    U1:and_2 port map(A,B,Carry);
    U2:xor_2 port map(A,B,Sum);
END a;
```

and\_2

```
library ieee;

    use ieee.std_logic_1164.all;

    entity and_2 is

        port ( A,B  :in std_logic;

              Carry :out std_logic);
```

```
end or_2;
```

```
ARCHITECTURE a OF or_2 IS
```

```
begin
```

```
    Carry <= A and B;
```

```
end a;
```

xor\_2

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
entity or_2 is
```

```
port ( A,B   :in std_logic;
```

```
       Sum    :out std_logic);
```

```
end or_2;
```


```
ARCHITECTURE a OF or_2 IS
```


```
begin
```

```
    Sum<=A xor B;
```

```
end a;
```

模擬結果:

 

 

## 第二題

■ 問題：利用階層式設計實現一個 4-bit 加法器(add\_4\_bits.vhd)

(1-bit 加法器: add\_1\_bit.vhd)。

程式碼: add\_4\_bits

```
library IEEE;
use IEEE.std_logic_1164.all;

entity add_4_bits is
port ( A: in std_logic_vector(3 DOWNTO 0);
      B: in std_logic_vector(3 DOWNTO 0);
      C: in std_logic;
      Sum: out std_logic_vector(3 DOWNTO 0);
      Carry: out std_logic );
end add_4_bits;

ARCHITECTURE a OF add_4_bits IS

    component add_1_bit
        port ( A,B,C :in std_logic;
              Sum,Carry : out std_logic );
    end component;

    signal s1,s2,s3 :std_logic;

BEGIN

    U1:add_1_bit port map(C,A(0),B(0),s1,Sum(0));
    U2:add_1_bit port map(s1,A(1),B(1),s2,Sum(1));
    U3:add_1_bit port map(s2,A(2),B(2),s3,Sum(2));
```

```
U4:add_1_bit port map(s3,A(3),B(3),Carry,Sum(3));
```

```
END a;
```

```
add_1_bit
```

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.all;
```

```
ENTITY add_1_bit IS
```

```
PORT ( A,B,C : IN STD_LOGIC;
```

```
Sum,carry : out STD_LOGIC);
```

```
END add_1_bit;
```

```
ARCHITECTURE a OF add_1_bit IS
```

```
component h_adder
```

```
port ( A,B :in std_logic;
```

```
Sum,Carry : out std_logic );
```

```
end component;
```

```
component or_2
```

```
port ( A,B :in std_logic;
```

```
Carry :out std_logic );
```

```
end component;
```

```
signal s1,s2,s3 :std_logic;
```

```
BEGIN
```

```
U1:h_adder port map(A,B,s1,s3);
```

```
U2:h_adder port map(s1,C,sum,s2);
```

```
U3:or_2 port map(s2,s3,carry);
```

**END a;**

**or\_2**

```
library ieee;

    use ieee.std_logic_1164.all;

    entity or_2 is

        port ( A,B    :in std_logic;

               Carry    :out std_logic);

    end or_2;


    ARCHITECTURE a OF or_2 IS

        begin

            Carry<=A or B;

        end a;
```

**實 驗 結 果 :**

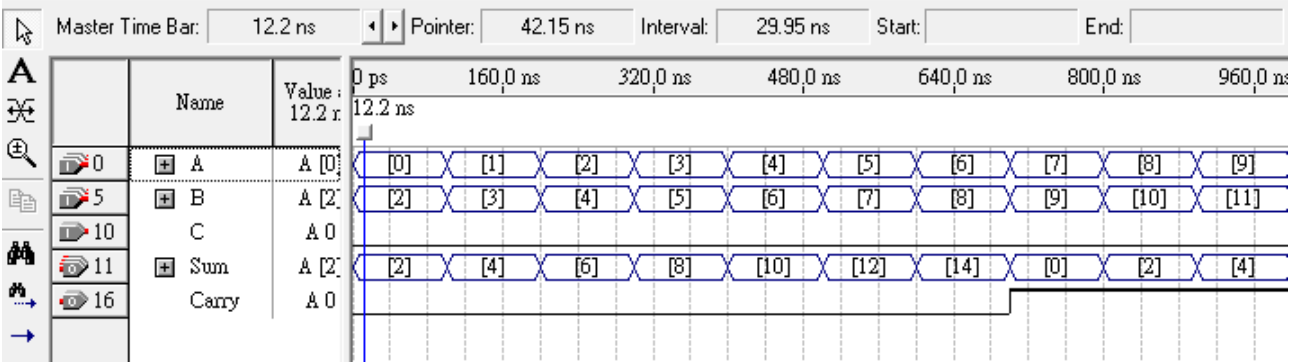

### 第三題

問題：以 5 個四對一的多工器實現一個十六對一的多工器。

程式碼: mux16to1c

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

ENTITY mux16to1c IS
PORT (  D : IN STD_LOGIC_vector(0 to 15);
        S : IN  STD_LOGIC_vector(3 downto 0);
        Y : OUT STD_LOGIC);
END mux16to1c ;

ARCHITECTURE a OF mux16to1c IS
component mux4_1 is
port ( d0,d1,d2,d3 :in std_logic;
        S1,S0      :in std_logic;
        Y           :out std_logic );
end component;
signal m :std_logic_vector(0 to 3);
BEGIN

    U1:mux4_1 port map(D(0),D(1),D(2),D(3),S(1),S(0),m(0));
    U2:mux4_1 port map(D(4),D(5),D(6),D(7),S(1),S(0),m(1));
    U3:mux4_1 port map(D(8),D(9),D(10),D(11),S(1),S(0),m(2));
    U4:mux4_1 port map(D(12),D(13),D(14),D(15),S(1),S(0),m(3));
```



```
U5:mux4_1 port map(m(0),m(1),m(2),M(3),S(3),S(2),Y);
```

```
END a;
```

```
mux4_1
```

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
entity mux4_1 is
```

```
port ( d0,d1,d2,d3 :in std_logic;
```

```
       S1,S0 :in std_logic;
```

```
       Y      :out std_logic);
```

```
end mux4_1;
```

```
ARCHITECTURE a OF mux4_1 IS
```

```
begin
```

```
    Y <= ((not S1)and (not S0)and d0)
```

```
        or((not S1)and S0 and d1)
```

```
        or (S1 and (not S0)and d2)
```

```
        or (S1 and S0 and d3);
```

```
end a;
```

實 驗 結 果 :

